

Logic Design


EECS101001

Lab 2: Applications of Multiplexer – Report

104021215 熊磊

 1. Foreword


This Lab is trying to use Multiplexer (or Selector) to select the module by **Sel** with input **A**, **B**, and output is **Out**, **Ovf**.



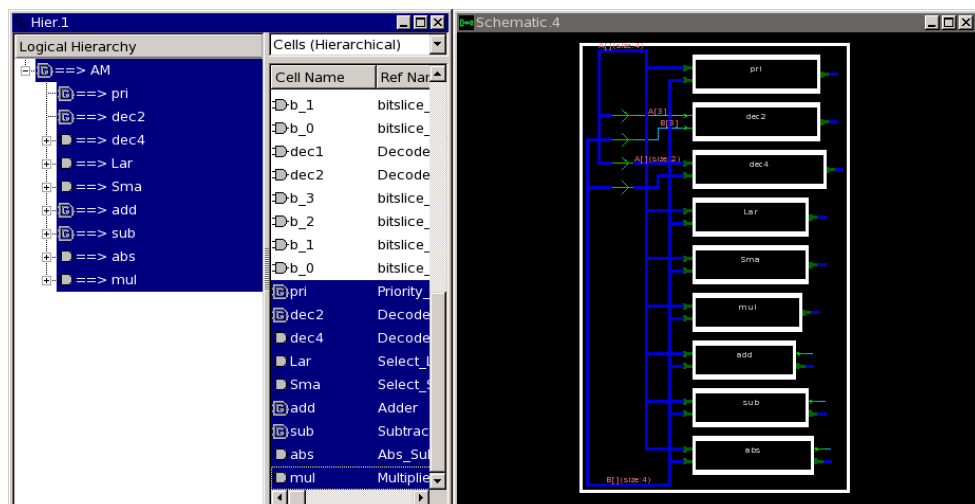2. Implementation Details and Designs

- Multiplexer

I use **always block** to implement the Multiplexer. The code is too long to show here, one can check **AM.v** in line #25~#109. Below is the image created by Design Vision.



Hence, we need to implement each module for each module.

- [0000] Priority Encoder

First I easily combine the two inputs **a**, **b** to **wire[7:0]ab**.

Then one can get the result of priority encoder by assign method check the bit from MSB to LSB one by one.

```

113 module Priority_Encoder(out, a, b);
114     // input with higher priority will take place
115     input wire [3:0]a,b;
116     output [2:0]out;
117
118     wire [7:0]ab;
119     assign ab = {a[3:0],b[3:0]};
120
121     assign out = (ab[7] == 1'b1) ? 3'b111:
122                 (ab[6] == 1'b1) ? 3'b110:
123                 (ab[5] == 1'b1) ? 3'b101:
124                 (ab[4] == 1'b1) ? 3'b100:
125                 (ab[3] == 1'b1) ? 3'b011:
126                 (ab[2] == 1'b1) ? 3'b010:
127                 (ab[1] == 1'b1) ? 3'b001: 3'b000;
128 endmodule

```

- [0001]~[0111] A&B, A^B, A*B, A>>>1'b1, ..., A<<<1'b1

For these functions, without restrictions, I directly use Verilog built-in operation.

```


33 1: begin // A&B
34     Out = {12'b0,A&B};
35     Ovfl = 1'b0;
36 end
37
38 2: begin // A^B
39     Out = {12'b0,A^B};
40     Ovfl = 1'b0;
41 end
42
43 3: begin // A*B
44     Out = {8'b0,{4{A[3]},A}*{4{B[3]},B}};
45     Ovfl = 1'b0;
46 end
47
48 4: begin // A>>>1'b1
49     Out = {12'b0,{A>>>1'b1}};
50     Ovfl = 1'b0;
51 end
52
53 5: begin // A<<<1'b1
54     Out = {12'b0,{A<<<1'b1}};
55     Ovfl = 1'b0;
56 end
57
58 6: begin // A>>1'b1
59     Out = {12'b0,{A>>1'b1}};
60     Ovfl = 1'b0;
61 end
62
63 7: begin // A<<1'b1
64     Out = {12'b0,{A<<1'b1}};
65     Ovfl = 1'b0;

```

- [1000] 2-to-4 decoder

We need to use **only gate level** to implement 2-to-4 decoder, we first write down the truth table and draw a simple diagram below.

A ₀	A ₁	D ₀	D ₁	D ₂	D ₃
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

Therefore, we need four **and gate** and two **not gate**. The code is below.

```


129 module Decoder_2_to_4(out, a, b); // Only gate level
130     input a,b;
131     output [3:0] out;
132
133     wire not_a, not_b;
134
135     not (not_a, a), (not_b, b);
136     and (out[3],a,b), (out[2],a,not_b), (out[1],not_a,b), (out[0],not_a,not_b);
137 endmodule

```

- [1001] 4-to-16 decoder

By reusing 2-to-4 decoder, the idea is very simple, we can draw a diagram below.

A[3:2]	B[3:2]	Out
00	00	0000_0000_0000_0001
00	01	0000_0000_0000_0010
00	10	0000_0000_0000_0100
00	11	0000_0000_0000_1000
01	00	0000_0000_0001_0000
01	01	0000_0000_0010_0000
01	10	0000_0000_0100_0000
01	11	0000_0000_1000_0000
10	00	0000_0001_0000_0000
10	01	0000_0010_0000_0000
10	10	0000_0100_0000_0000
10	11	0000_1000_0000_0000
11	00	0001_0000_0000_0000
11	01	0010_0000_0000_0000
11	10	0100_0000_0000_0000
11	11	1000_0000_0000_0000

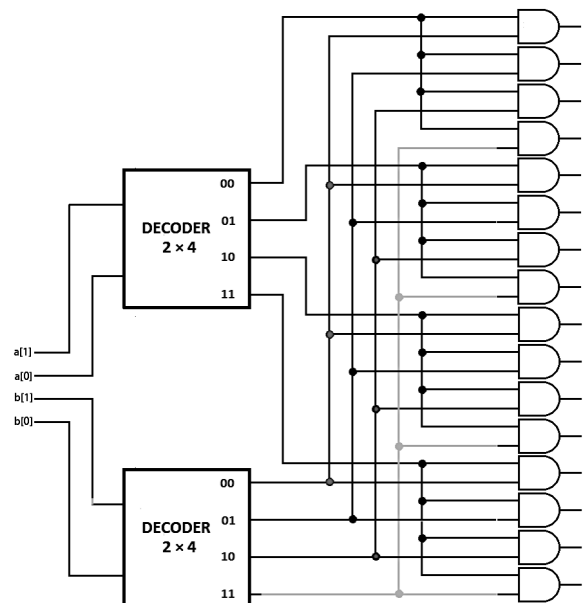


Therefore, we need sixteen **and gate** and two **2-4 Decoder**. The code is below.

```

139 module Decoder_4_to_16(out, a, b); // Only gate level
140     input [1:0] a, b;
141     output [15:0] out;
142
143     wire [3:0] x, y;
144
145     Decoder_2_to_4 dec1(x, a[1], a[0]);
146     Decoder_2_to_4 dec2(y, b[1], b[0]);
147
148     and (out[0], x[0], y[0]), (out[1], x[0], y[1]), (out[2], x[0], y[2]),
149         (out[3], x[0], y[3]), and4 (out[4], x[1], y[0]), (out[5], x[1], y[1]),
150         (out[6], x[1], y[2]), (out[7], x[1], y[3]), (out[8], x[2], y[0]),
151         (out[9], x[2], y[1]), (out[10], x[2], y[2]), (out[11], x[2], y[3]),
152         (out[12], x[3], y[0]), (out[13], x[3], y[1]), (out[14], x[3], y[2]),
153         (out[15], x[3], y[3]);
154 endmodule

```

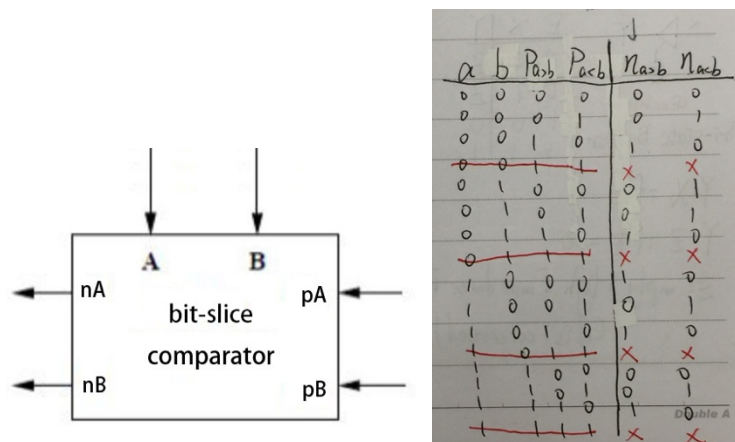- [1010]~[1011] Select the larger number, Select the smaller number
[Design Bit Slice - Comparator]



nA is equivalent to (A+pA)&pB'

nB is equivalent to (B+pB)&pA'


If nA is 1, A>B; if nB is 1, B>A.

```

156 module bitslice(out, pa, pb, a, b);
157     input pa, pb, a, b;
158     output [1:0] out;
159
160     wire not_a, not_b, not_pa, not_pb, or_a, or_b;
161
162     not (not_pa, pa), (not_pb, pb);
163     or (or_a, a, pa), (or_b, b, pb);
164     and (out[1], or_a, not_pb), (out[0], or_b, not_pa);
165 endmodule

```

 So, we can use Comparator repeatedly, like this. For example.
Select the larger number. We just have to check if nA is 1.



```

167 module Select_Large(out, a, b); // Design bit slice
168     input [3:0] a, b;
169     output [3:0] out;
170
171     wire [1:0] nab0, nab1, nab2, nab3, nab4;
172     assign nab4 = 2'b0;
173     bitslice b_3(nab3, nab4[1], nab4[0], a[3], b[3]);
174     bitslice b_2(nab2, nab3[1], nab3[0], a[2], b[2]);
175     bitslice b_1(nab1, nab2[1], nab2[0], a[1], b[1]);
176     bitslice b_0(nab0, nab1[1], nab1[0], a[0], b[0]);
177
178     assign out = (nab0[1]) ? a : b;
179 endmodule

```

On the other hand, Select the smaller number, we can just choose the one not the large.

```


181 module Select_Small(out, a, b); // Design bit slice
182   input [3:0] a,b;
183   output [3:0] out;
184
185   wire [1:0] nab0,nab1,nab2,nab3,nab4;
186   assign nab4 = 2'b0;
187   bitslice b_3(nab3, nab4[1], nab4[0], a[3], b[3]);
188   bitslice b_2(nab2, nab3[1], nab3[0], a[2], b[2]);
189   bitslice b_1(nab1, nab2[1], nab2[0], a[1], b[1]);
190   bitslice b_0(nab0, nab1[1], nab1[0], a[0], b[0]);
191
192   assign out = (!nab0[1]) ? a : b;
193 endmodule

```

- [1100] A+B

[Design Bit Slice – Full Adder]

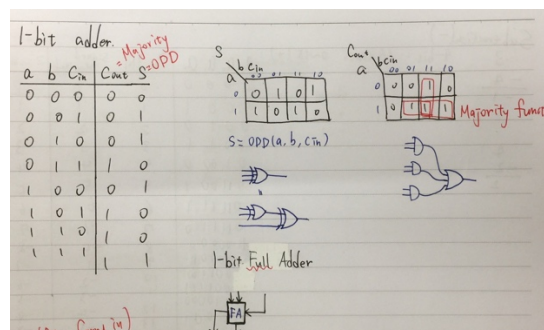Here we first analyze **Cout** and **s**. By drawing a truth table and K-map, found that they are Majority function and ODD function respectively.




```

195 module Bit_Adder(cout, s, a, b, cin); // Design bit slice
196   input a,b,cin;
197   output cout,s;
198
199   wire and0,and1,and2;
200   xor (s,a,b,cin); // ODD function
201
202   and (and0,a,b),(and1,b,cin),(and2,a,cin);
203   or (cout,and0,and1,and2);
204 endmodule

```

 Now, we can use Full adder repeatedly for four-digits input to implement **Adder**. To detect overflow, using an **xor** gate at the last Full Adder.



```

206 module Adder(out, ovf, a, b);
207   input [3:0] a,b;
208   output [3:0] out;
209   output ovf;
210
211   wire [3:0] cout,c,d;
212
213   Bit_Adder ad3(cout[0], out[0], a[0], b[0], 1'b0);
214   Bit_Adder ad2(cout[1], out[1], a[1], b[1], cout[0]);
215   Bit_Adder ad1(cout[2], out[2], a[2], b[2], cout[1]);
216   Bit_Adder ad0(cout[3], out[3], a[3], b[3], cout[2]);
217
218   xor (ovf, cout[3], cout[2]); //Overflow detection
219 endmodule

```

- [1101] A-B

[Reuse Adder]

It's easy to implement Subtractor by reusing Adder. We just change the problem A-B to the problem A+(-B). Just like line #227 below.

```

221 module Subtractor(out, ovf, a, b); // Reuse adder
222     input [3:0] a,b;
223     output [3:0] out;
224     output ovf;
225
226     wire [3:0] b2;
227     assign b2[3:0] = (~b[3:0] + 1'b1);
228     Adder add(out, ovf, a, b2);
229 endmodule

```

- [1110] | A-B |

[Reuse Subtractor]

If overflow, we don't care about the output.

The only step we need to care is to make sure the output is positive. Therefore, convert to positive if it's negative. As show in Line #239.

```


231 module Abs_Subtractor(out, ovf, a, b); // Reuse Subtractor
232     input [3:0] a,b;
233     output [3:0] out;
234     output ovf;
235
236     wire [3:0] tmp;
237
238     Subtractor sub(tmp, ovf, a, b);
239     assign out = (tmp[3]) ? (~tmp[3:0] + 1'b1) : tmp;
240
241 endmodule

```

- [1111] A*B

[Only Gate Level]

 I use array Multiplier to implement. The diagram is below. It's hard to say in text, but the main idea is to reuse Full Adder(made by gate level) to control bit slice, and use **and** gate to do bit-multiplying.



```

243 module Multiplier(out, a, b); // Only gate level
244     input [3:0] a,b;
245     output [7:0] out;
246
247     wire c1,c2,c3,c4,c5,c6,c7,c8,c9,c10,c11,c12,c13,c14,
248           d1,d2,d3,d4,d5,d6,d7,
249           e1,e2,e3,e4,e5,e6,e7,
250           f1,f2,f3,f4;
251
252     and (c1,b[3],a[1]), (c2,b[2],a[2]), (c3,b[1],a[3]),
253          (c4,b[3],a[0]), (c5,b[2],a[1]), (c6,b[1],a[2]),
254          (c7,b[2],a[0]), (c8,b[1],a[1]), (c9,b[0],a[2]),
255          (c10,b[1],a[0]), (c11,b[0],a[1]), (out[0],b[0],a[0]),
256          (c12,b[2],a[3]), (c13,b[3],a[2]), (c14,b[0],a[3]),
257          (f1,b[3],a[3]);
258
259     Bit_Adder bitAdder0(d1,d2,c1,c2,c3);
260     Bit_Adder bitAdder1(d3,d4,c4,c5,c6);
261     Bit_Adder bitAdder2(d5,d6,c7,c8,c9);
262     Bit_Adder bitAdder3(d7,out[1],c10,c11,1'b0);
263
264     Bit_Adder bitAdder4(e1,e2,c12,c13,d1);
265     Bit_Adder bitAdder5(e3,e4,d2,d3,e5);
266     Bit_Adder bitAdder6(e5,e6,d4,c14,d5);
267     Bit_Adder bitAdder7(e7,out[2],d6,d7,1'b0);
268     Bit_Adder bitAdder8(out[7],out[6],f1,e1,f2);
269
270     Bit_Adder bitAdder9(f2,out[5],e2,e3,f3);
271     Bit_Adder bitAdder10(f3,out[4],e4,1'b0,f4);
272     Bit_Adder bitAdder11(f4,out[3],e6,e7,1'b0);
273 endmodule

```

3. Simulation Result

[Before Synthesis]

```
test_case No. 1: A = 0000, B = 0001, Sel = 0000, Out = 0000000000000000, Ovf = 0
test_case No. 2: A = 0001, B = 0110, Sel = 0000, Out = 0000000000000100, Ovf = 0
test_case No. 3: A = 0111, B = 0001, Sel = 0001, Out = 0000000000000001, Ovf = 0
test_case No. 4: A = 0001, B = 0110, Sel = 0001, Out = 0000000000000000, Ovf = 0
test_case No. 5: A = 0111, B = 0001, Sel = 0010, Out = 0000000000000110, Ovf = 0
test_case No. 6: A = 0001, B = 0110, Sel = 0010, Out = 0000000000000111, Ovf = 0
test_case No. 7: A = 0111, B = 0011, Sel = 0011, Out = 0000000000010101, Ovf = 0
test_case No. 8: A = 0001, B = 0110, Sel = 0011, Out = 0000000000000110, Ovf = 0
test_case No. 9: A = 0111, B = 0000, Sel = 0100, Out = 0000000000000011, Ovf = 0
test_case No. 10: A = 0001, B = 0000, Sel = 0100, Out = 0000000000000000, Ovf = 0
test_case No. 11: A = 0111, B = 0000, Sel = 0101, Out = 0000000000001110, Ovf = 0
test_case No. 12: A = 0001, B = 0000, Sel = 0101, Out = 0000000000000010, Ovf = 0
test_case No. 13: A = 0111, B = 0000, Sel = 0110, Out = 0000000000000011, Ovf = 0
test_case No. 14: A = 0001, B = 0000, Sel = 0110, Out = 0000000000000000, Ovf = 0
test_case No. 15: A = 0111, B = 0000, Sel = 0111, Out = 0000000000000110, Ovf = 0
test_case No. 16: A = 0101, B = 0000, Sel = 0111, Out = 0000000000000101, Ovf = 0
test_case No. 17: A = 0000, B = 0000, Sel = 1000, Out = 0000000000000001, Ovf = 0
test_case No. 18: A = 0000, B = 1000, Sel = 1000, Out = 0000000000000010, Ovf = 0
test_case No. 19: A = 0000, B = 0000, Sel = 1001, Out = 0000000000000001, Ovf = 0
test_case No. 20: A = 0000, B = 1000, Sel = 1001, Out = 0000000000000100, Ovf = 0
test_case No. 21: A = 0100, B = 0011, Sel = 1010, Out = 0000000000000010, Ovf = 0
test_case No. 22: A = 0000, B = 1000, Sel = 1010, Out = 0000000000000100, Ovf = 0
test_case No. 23: A = 0100, B = 0011, Sel = 1011, Out = 0000000000000011, Ovf = 0
test_case No. 24: A = 0000, B = 1000, Sel = 1011, Out = 0000000000000000, Ovf = 0
test_case No. 25: A = 0100, B = 0011, Sel = 1100, Out = 0000000000000111, Ovf = 0
test_case No. 26: A = 0000, B = 1000, Sel = 1100, Out = 1111111111110000, Ovf = 0
test_case No. 27: A = 0100, B = 0011, Sel = 1101, Out = 0000000000000001, Ovf = 0
test_case No. 28: A = 0000, B = 1100, Sel = 1101, Out = 0000000000000100, Ovf = 0
test_case No. 29: A = 0100, B = 0011, Sel = 1110, Out = 0000000000000001, Ovf = 0
test_case No. 30: A = 0000, B = 0100, Sel = 1110, Out = 0000000000000100, Ovf = 0
test_case No. 31: A = 1111, B = 0100, Sel = 1110, Out = 0000000000000101, Ovf = 0
test_case No. 32: A = 1100, B = 0101, Sel = 1110, Out = 0000000000000111, Ovf = 1
All Correct.

Test bonus...

Bonus No. 33: A = 0111, B = 0011, Sel = 1111, Out = 0000000000010101, Ovf = 0
Bonus No. 34: A = 0001, B = 0110, Sel = 1111, Out = 0000000000000110, Ovf = 0

Get bonus.
```

[Run Synthesis]

```
test_case No. 1: A = 0000, B = 0001, Sel = 0000, Out = 0000000000000000, Ovf = 0
test_case No. 2: A = 0001, B = 0110, Sel = 0000, Out = 0000000000000100, Ovf = 0
test_case No. 3: A = 0111, B = 0001, Sel = 0001, Out = 0000000000000001, Ovf = 0
test_case No. 4: A = 0001, B = 0110, Sel = 0001, Out = 0000000000000000, Ovf = 0
test_case No. 5: A = 0111, B = 0001, Sel = 0010, Out = 0000000000000110, Ovf = 0
test_case No. 6: A = 0001, B = 0110, Sel = 0010, Out = 0000000000000111, Ovf = 0
test_case No. 7: A = 0111, B = 0011, Sel = 0011, Out = 0000000000010101, Ovf = 0
test_case No. 8: A = 0001, B = 0110, Sel = 0011, Out = 0000000000000110, Ovf = 0
test_case No. 9: A = 0111, B = 0000, Sel = 0100, Out = 0000000000000011, Ovf = 0
test_case No. 10: A = 0001, B = 0000, Sel = 0100, Out = 0000000000000000, Ovf = 0
test_case No. 11: A = 0111, B = 0000, Sel = 0101, Out = 0000000000000110, Ovf = 0
test_case No. 12: A = 0001, B = 0000, Sel = 0101, Out = 0000000000000010, Ovf = 0
test_case No. 13: A = 0111, B = 0000, Sel = 0110, Out = 0000000000000011, Ovf = 0
test_case No. 14: A = 0001, B = 0000, Sel = 0110, Out = 0000000000000000, Ovf = 0
test_case No. 15: A = 0111, B = 0000, Sel = 0111, Out = 0000000000000110, Ovf = 0
test_case No. 16: A = 0101, B = 0000, Sel = 0111, Out = 0000000000000101, Ovf = 0
test_case No. 17: A = 0000, B = 0000, Sel = 1000, Out = 0000000000000001, Ovf = 0
test_case No. 18: A = 0000, B = 1000, Sel = 1000, Out = 0000000000000010, Ovf = 0
test_case No. 19: A = 0000, B = 0000, Sel = 1001, Out = 0000000000000001, Ovf = 0
test_case No. 20: A = 0000, B = 1000, Sel = 1001, Out = 0000000000000100, Ovf = 0
test_case No. 21: A = 0100, B = 0011, Sel = 1010, Out = 0000000000000010, Ovf = 0
test_case No. 22: A = 0000, B = 1000, Sel = 1010, Out = 0000000000000100, Ovf = 0
test_case No. 23: A = 0100, B = 0011, Sel = 1011, Out = 0000000000000011, Ovf = 0
test_case No. 24: A = 0000, B = 1000, Sel = 1011, Out = 0000000000000000, Ovf = 0
test_case No. 25: A = 0100, B = 0011, Sel = 1100, Out = 0000000000000111, Ovf = 0
test_case No. 26: A = 0000, B = 1000, Sel = 1100, Out = 1111111111110000, Ovf = 0
test_case No. 27: A = 0100, B = 0011, Sel = 1101, Out = 0000000000000001, Ovf = 0
test_case No. 28: A = 0000, B = 1100, Sel = 1101, Out = 0000000000000100, Ovf = 0
test_case No. 29: A = 0100, B = 0011, Sel = 1110, Out = 0000000000000001, Ovf = 0
test_case No. 30: A = 0000, B = 0100, Sel = 1110, Out = 0000000000000100, Ovf = 0
test_case No. 31: A = 1111, B = 0100, Sel = 1110, Out = 0000000000000101, Ovf = 0
test_case No. 32: A = 1100, B = 0101, Sel = 1110, Out = 0000000000000111, Ovf = 1
All Correct.

Test bonus...

Bonus No. 33: A = 0111, B = 0011, Sel = 1111, Out = 0000000000010101, Ovf = 0
Bonus No. 34: A = 0001, B = 0110, Sel = 1111, Out = 0000000000000110, Ovf = 0

Get bonus.

Simulation complete via $finish(1) at time 680 NS + 0
./AM_tb.v:89 $finish;
```

4. Report Area

```
*****
Report : area
Design : AM
Version : K-2015.06-SP1
Date : Sat Mar 30 15:15:39 2019
*****

Information: Updating design information... (UID=85)
Library(s) Used:

slow (File: /theda21_2/CBDD_IC_Context/cur/SynopsysDC/db/slow.db)

Number of ports: 396
Number of nets: 695
Number of cells: 371
Number of combinational cells: 318
Number of sequential cells: 6
Number of macros/black boxes: 0
Number of buf/inv: 49
Number of references: 29

Combinational area: 2824.473582
Buf/Inv area: 166.345197
Noncombinational area: 0.000000
Macro/Black Box area: 0.000000
Net Interconnect area: undefined (No wire load specified)

Total cell area: 2824.473582
Total area: undefined
1
```

5. Encountered Problems and Solving

- Cannot using **assign** in **always block**.
- Cannot instantiate **module** in **always block**.
- Reg can only using in **always block**.
- We can use big parentheses {} to do sign extension or merge.
e.g. {a, b}, {12'b0, a&b}, {8'b0, {{4{a[3]}}, a}*{{4{b[3]}},b}}...
Amazing!!
- To reduce the coding time, drawing the diagram is really helpful!

6. Questions

- Why we can ignore the function name to built-in module but cannot ignore in my own module?

e.g.

```
and    (and0,a,b);    legal!  
my_and (and0,a,b);    illegal!  
my_and and_0(and0,a,b); legal!
```

- What is meaning of **combinational “area”** in report_area.txt?

7. Impression and Experience

Before I start this lab, I think this is a really tough, cause I have to implement totally 16 function. However, most of them are easily. By reusing the module, can reduce workload significantly!! I think, however, the most difficult one is bonus one, since there are lots of gate have to be connected...

Thank TAs for helping us and teaching us. Take care:-)